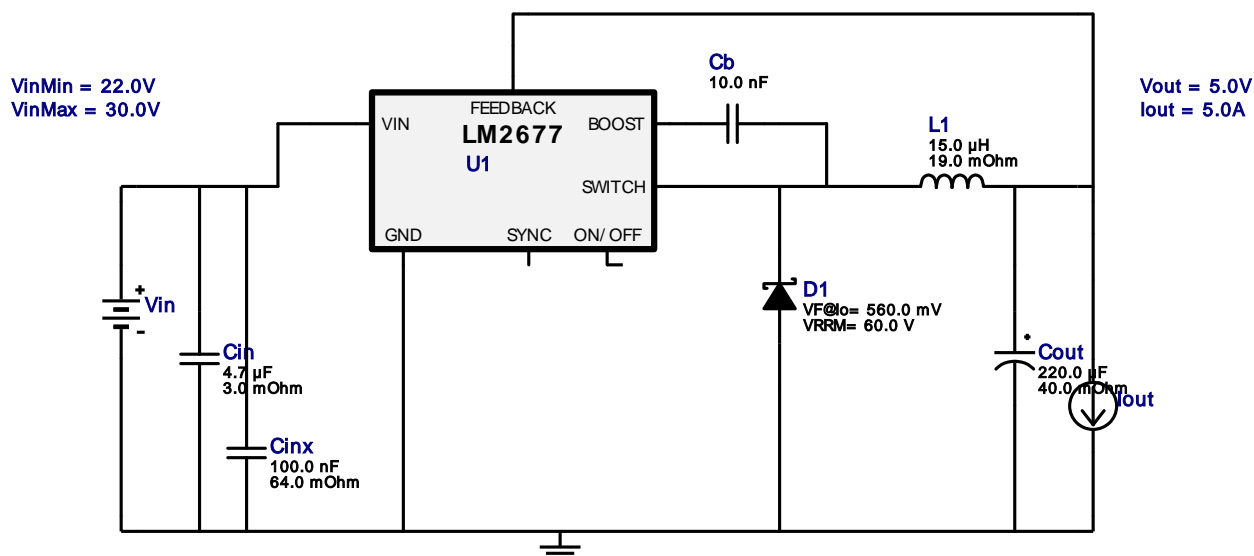







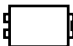
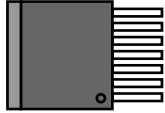
WEBENCH® Design Report







Design : 4270138/2 LM2677SX-5.0/NOPB
LM2677SX-5.0/NOPB 22.0V-30.0V to 5.00V @ 5.0A















Electrical BOM


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cb	MuRata	GRM216R71H103KA01D Series= X7R	Cap= 10.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	 0805 7 mm ²
2.	Cin	MuRata	GRM31CR71H475KA12L Series= X7R	Cap= 4.7 uF ESR= 3.0 mOhm VDC= 50.0 V IRMS= 4.98 A	1	\$0.22	 1206 11 mm ²
3.	Cinx	Kemet	C0805C104K5RACTU Series= X7R	Cap= 100.0 nF ESR= 64.0 mOhm VDC= 50.0 V IRMS= 1.64 A	1	\$0.01	 0805 7 mm ²
4.	Cout	Panasonic	10TPB220ML Series= ?	Cap= 220.0 uF ESR= 40.0 mOhm VDC= 10.0 V IRMS= 2.0 A	1	\$0.65	 7343-31 59 mm ²
5.	D1	Diodes Inc.	PDS760-13	Vf@Io= 560.0 mV VRRM= 60.0 V	1	\$0.60	 PowerDI5 50 mm ²
6.	L1	Coilcraft	MSS1210-153MEB	L= 15.0 µH DCR= 19.0 mOhm	1	\$0.81	 MSS1210 204 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
7.	U1	Texas Instruments	LM2677SX-5.0/NOPB	Switcher	1	\$2.25	 TS7B 199 mm ²

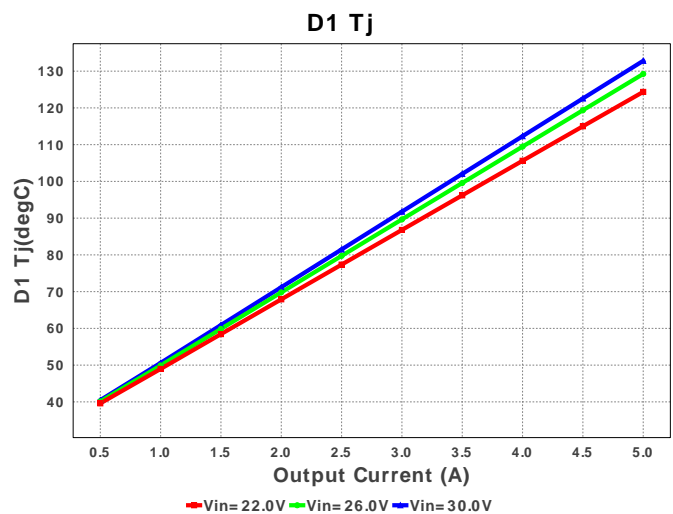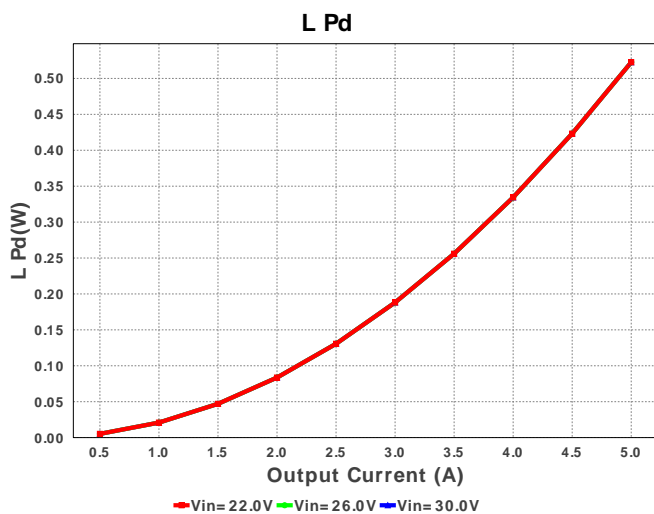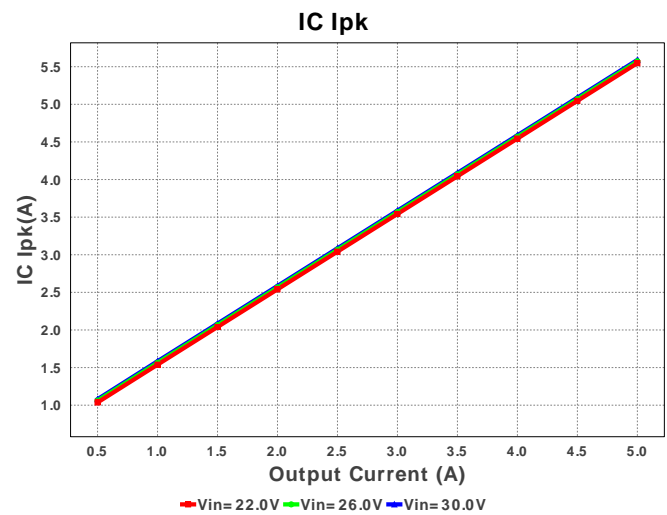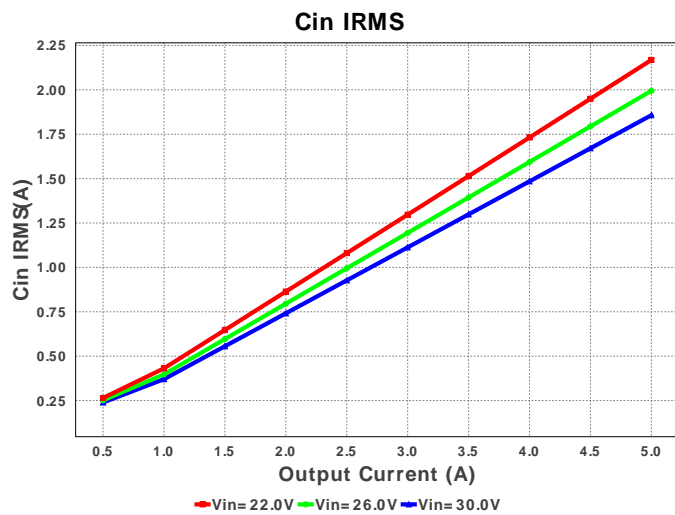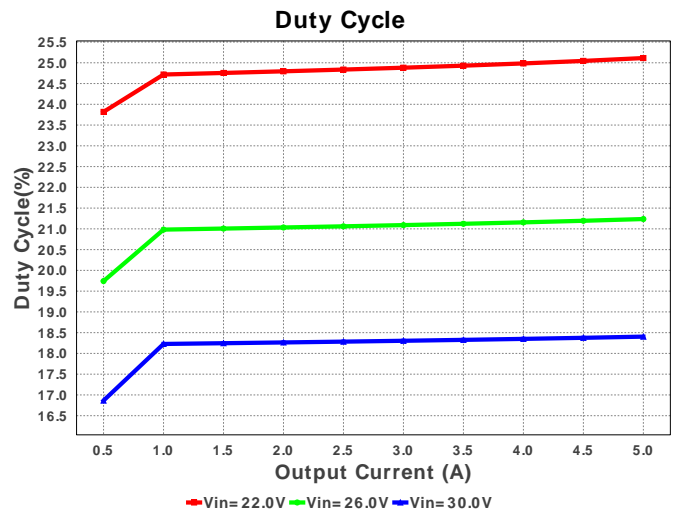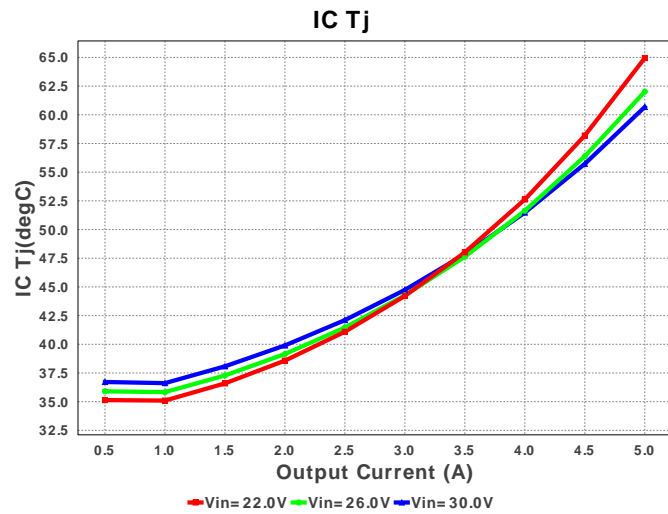

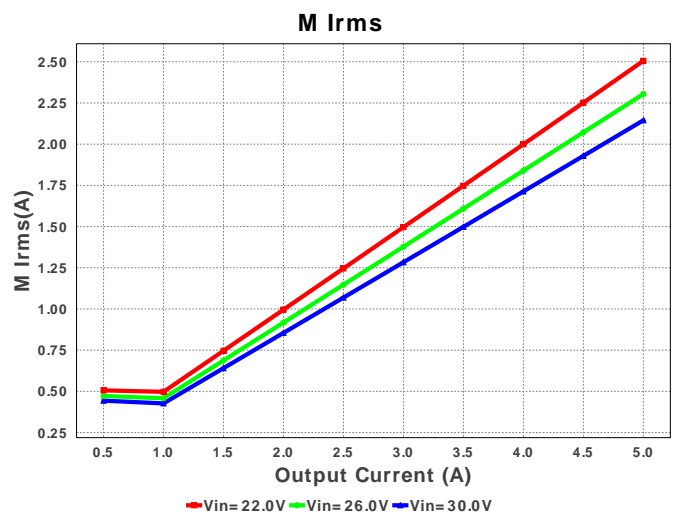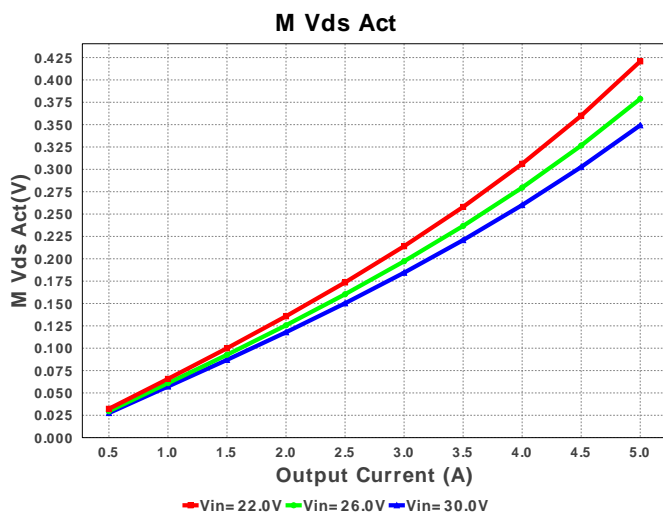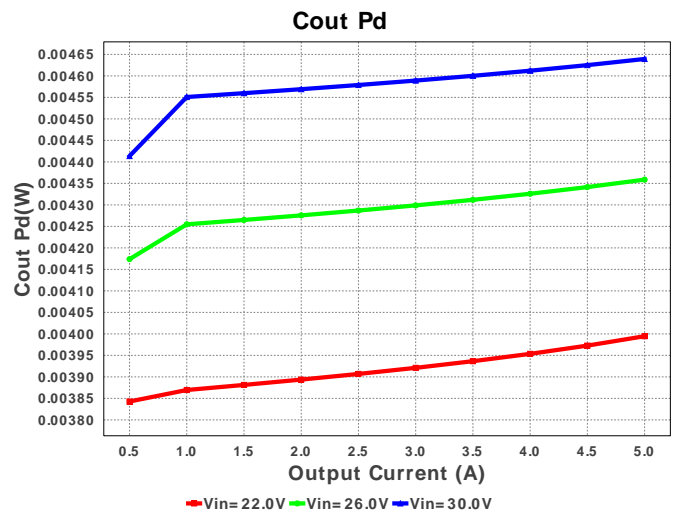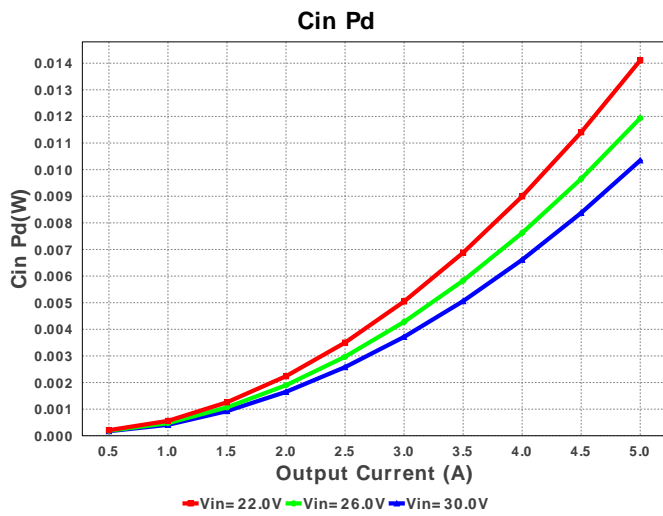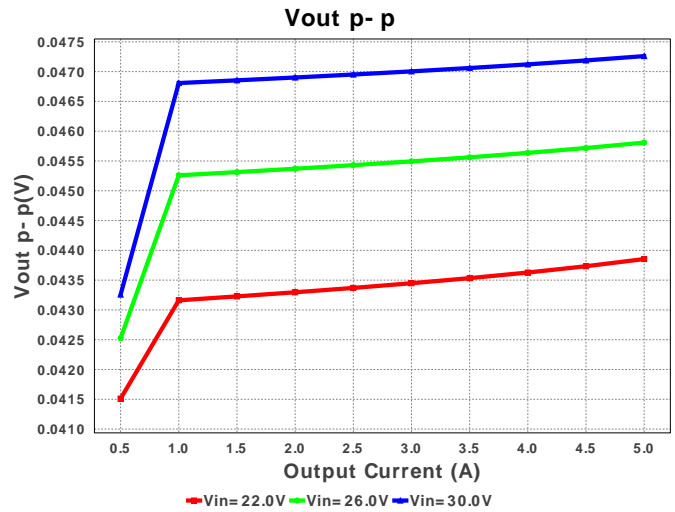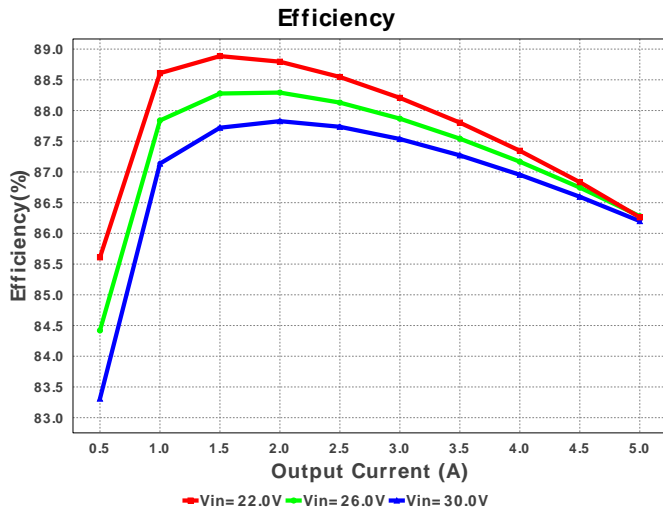

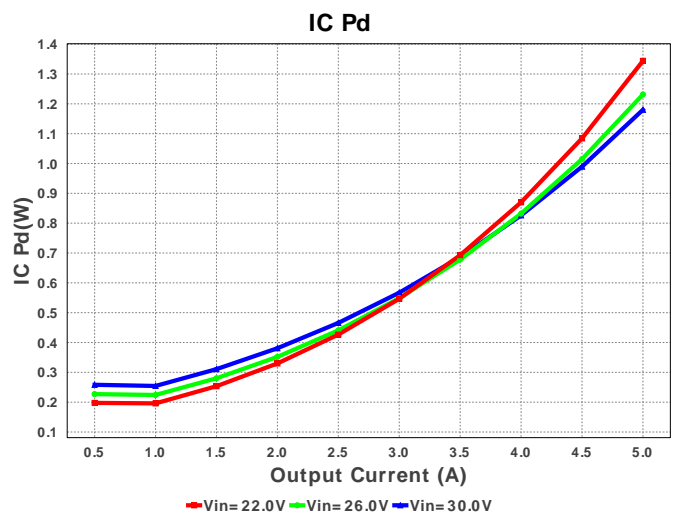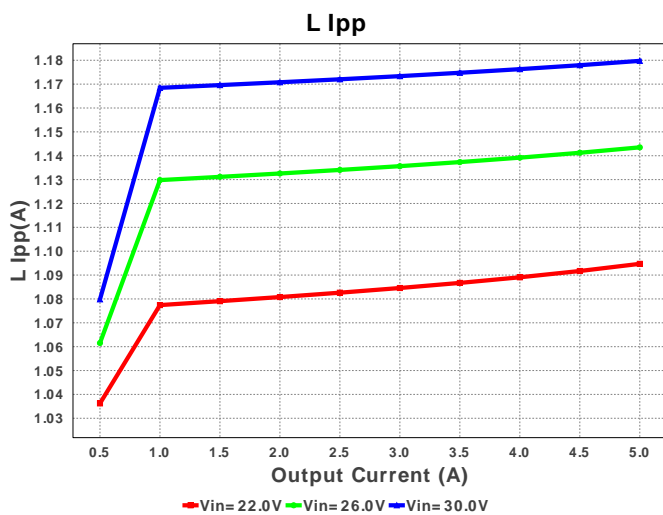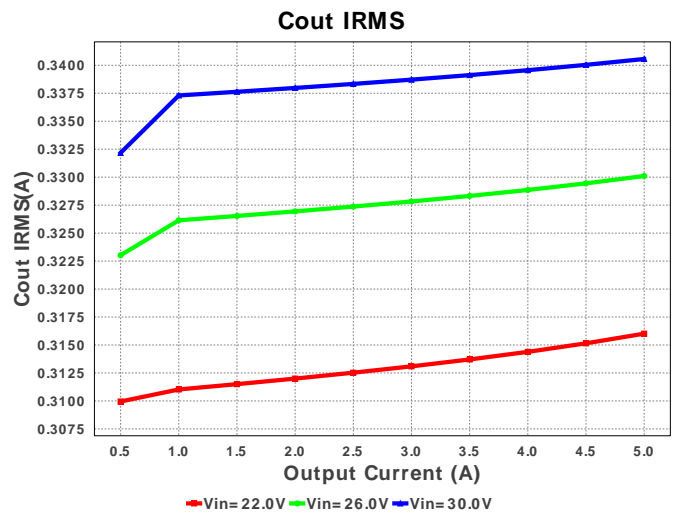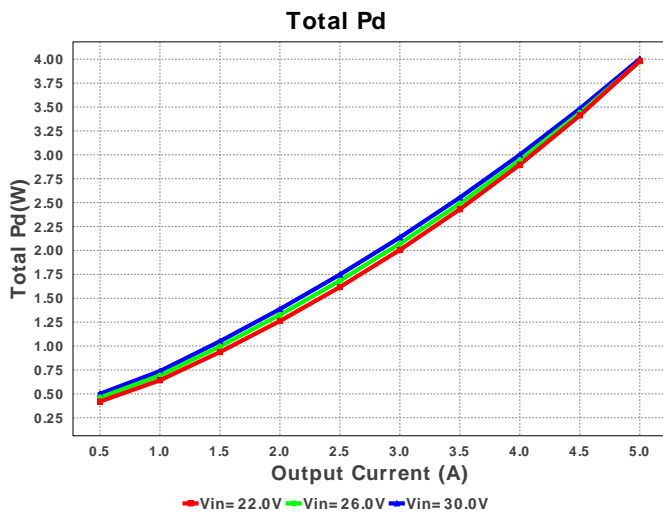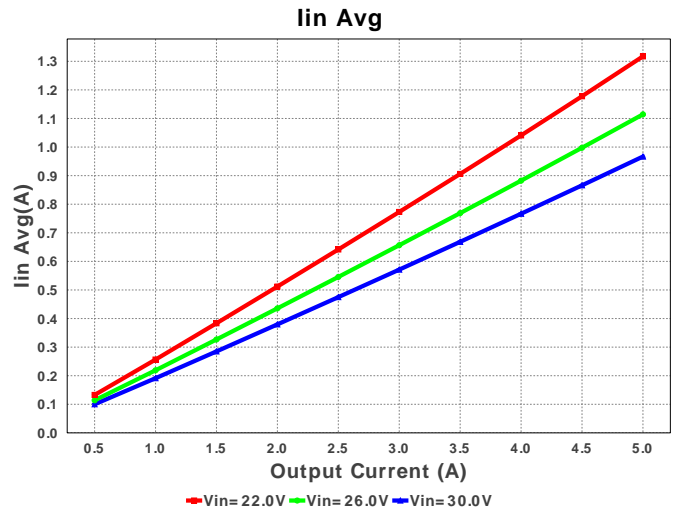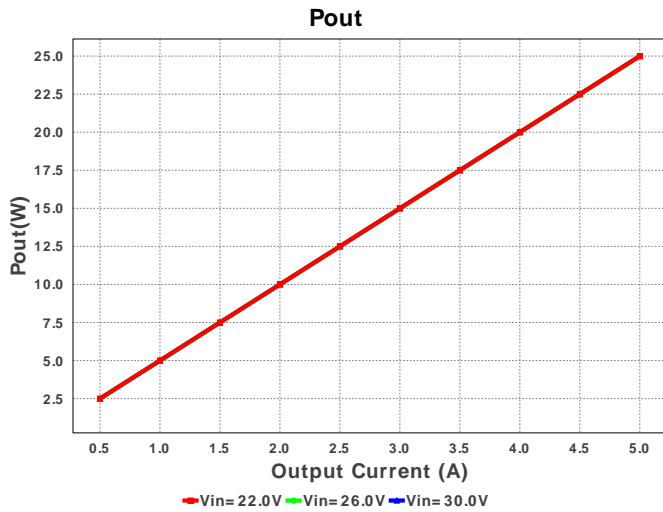

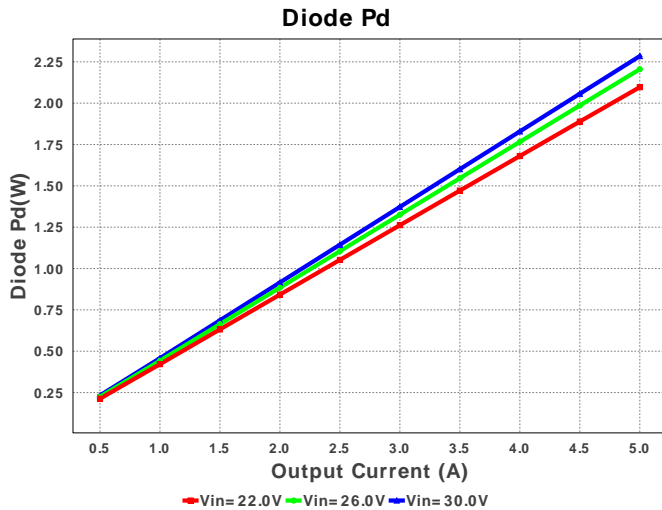

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	1.857 A	Current	Input capacitor RMS ripple current
2.	Cout IRMS	340.563 mA	Current	Output capacitor RMS ripple current
3.	IC Ipk	5.59 A	Current	Peak switch current in IC
4.	Iin Avg	966.74 mA	Current	Average input current
5.	L Ipp	1.18 A	Current	Peak-to-peak inductor ripple current
6.	M1 Irms	2.145 A	Current	Q lavg
7.	BOM Count	7	General	Total Design BOM count
8.	FootPrint	536.0 mm ²	General	Total Foot Print Area of BOM components
9.	Frequency	260.0 kHz	General	Switching frequency
10.	IC Tolerance	100.0 mV	General	IC Feedback Tolerance
11.	M Vds Act	349.245 mV	General	Voltage drop across the MosFET
12.	Pout	25.0 W	General	Total output power
13.	Total BOM	\$4.55	General	Total BOM Cost
14.	D1 Tj	132.811 degC	Op_Point	D1 junction temperature
15.	Vout OP	5.0 V	Op_Point	Operational Output Voltage
16.	Cross Freq	50.731 kHz	Op_point	Bode plot crossover frequency
17.	Duty Cycle	18.404 %	Op_point	Duty cycle
18.	Efficiency	86.2 %	Op_point	Steady state efficiency
19.	IC Tj	60.683 degC	Op_point	IC junction temperature
20.	ICThetaJA	26.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
21.	IOUT_OP	5.0 A	Op_point	Iout operating point
22.	Phase Marg	94.459 deg	Op_point	Bode Plot Phase Margin
23.	VIN_OP	30.0 V	Op_point	Vin operating point
24.	Vout p-p	47.26 mV	Op_point	Peak-to-peak output ripple voltage
25.	Cin Pd	10.348 mW	Power	Input capacitor power dissipation
26.	Cout Pd	4.639 mW	Power	Output capacitor power dissipation
27.	Diode Pd	2.285 W	Power	Diode power dissipation
28.	IC Pd	1.18 W	Power	IC power dissipation
29.	L Pd	522.5 mW	Power	Inductor power dissipation
30.	Total Pd	4.002 W	Power	Total Power Dissipation

Design Inputs

#	Name	Value	Description
1.	Iout	5.0	Maximum Output Current
2.	Iout1	5.0	Output Current #1
3.	VinMax	30.0	Maximum input voltage
4.	VinMin	22.0	Minimum input voltage
5.	Vout	5.0	Output Voltage
6.	Vout1	5.0	Output Voltage #1
7.	base_pn	LM2677	Base Product Number
8.	source	DC	Input Source Type
9.	Ta	30.0	Ambient temperature

Design Assistance

1. **LM2677** Product Folder : <http://www.ti.com/product/lm2677> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).